

S.No. : 93

NEC 4101

No. of Printed Pages : 06

Following Paper ID and Roll No. to be filled in your Answer Book.

PAPER ID : 43401

Roll
No.

--	--	--	--	--	--	--	--	--	--

B. Tech. Examination, 2024-25

(Odd Semester)

BASIC ELECTRONICS ENGINEERING

Time : Three Hours]

[Maximum Marks : 60

Note :- Attempt all questions.

SECTION-A

1. Attempt all parts of the following : $8 \times 1 = 8$
- (a) What are acceptor and donor impurities?
 - (b) What is the effect of temperature on the reverse current of a P-N-junction?
 - (c) What do you mean by ripple factor?
 - (d) The value of α for a transistor is 0.950. Find the value of β .

[P. T. O.]

- (e) Why BJT transistor is called current controlled device?
- (f) What is pinch-off voltage in a JFET?
- (g) What are the characteristic of an ideal op-amp?
- (h) Define I_{CBO} .

SECTION – B

2. Attempt any two parts of the following : $2 \times 6 = 12$
- (a) Describe the conditions established by forward and reverse-bias conditions on a PN-junction diode and how the resulting current is affected?
 - (b) A full wave bridge rectifier with 220V, 50 Hz sinusoidal input and turns ratio of 5 : 1 has a load resistance of 500Ω . Diode forward resistance is 20Ω . Determine :
 - (i) Mean or average load current
 - (ii) Rectification efficiency
 - (iii) Ripple factor
 - (c) Explain the basic construction and principle of operation of BJT.


- (d) Perform the following subtraction using 1's and 2's - complement method :

$$(42)_{10} - (32)_{10}$$


SECTION - C

Note :- Attempt all questions. Attempt any two parts from each questions. $8 \times 5 = 40$

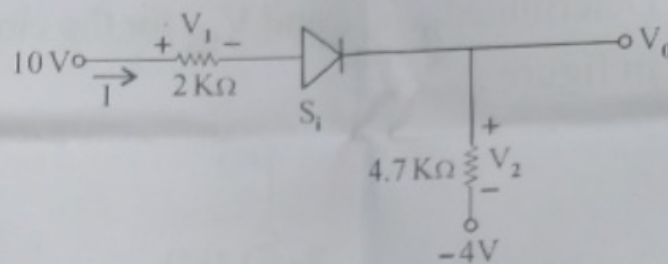3. (a) Determine I , V_1 , V_2 and V_0 for the circuit shown in figure :




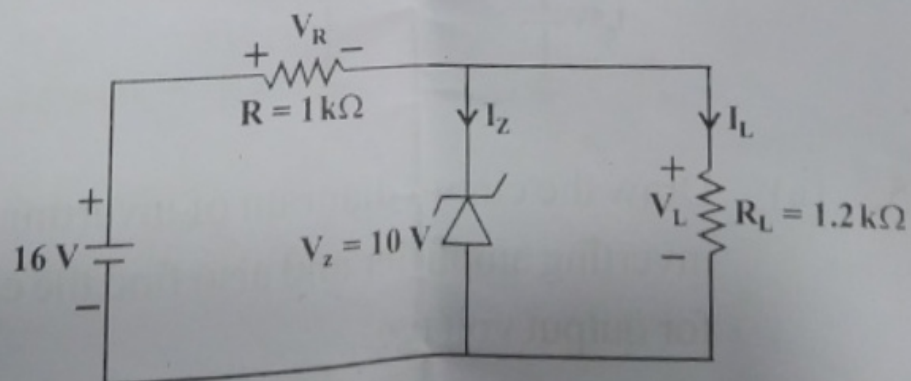- (b) Explain the working of centre-tapped full wave rectifier with neat circuit diagram and output waveform.
- (c) Explain the zener breakdown mechanism for the following circuit, find V_L , V_R , I_Z and I_L :




[P. T. O.]

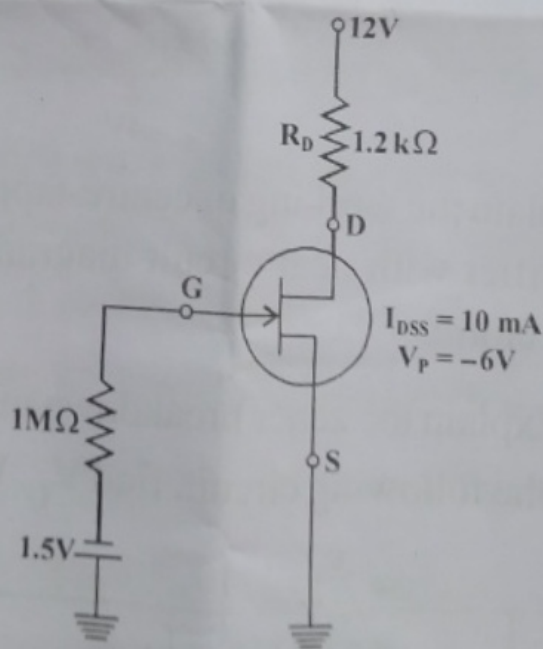4. (a) Explain the input and output characteristic of a transistor in CB configuration. Also derive the relationship between α and β .
- (b) For a transistor in common emitter configuration, the reverse leakage current is $21 \mu\text{A}$, whereas when the same transistor is connected in common-base configuration it reduces to $1.1 \mu\text{A}$. Calculate values α and β of the transistor.
- (c) Determine I_D , V_{GS} and V_{DS} for the circuit shown in figure :



5. (a) Draw the circuit diagram of inverting and non-inverting amplifier and also find the expression for output voltage.

(b) Find the output voltage V_0 :

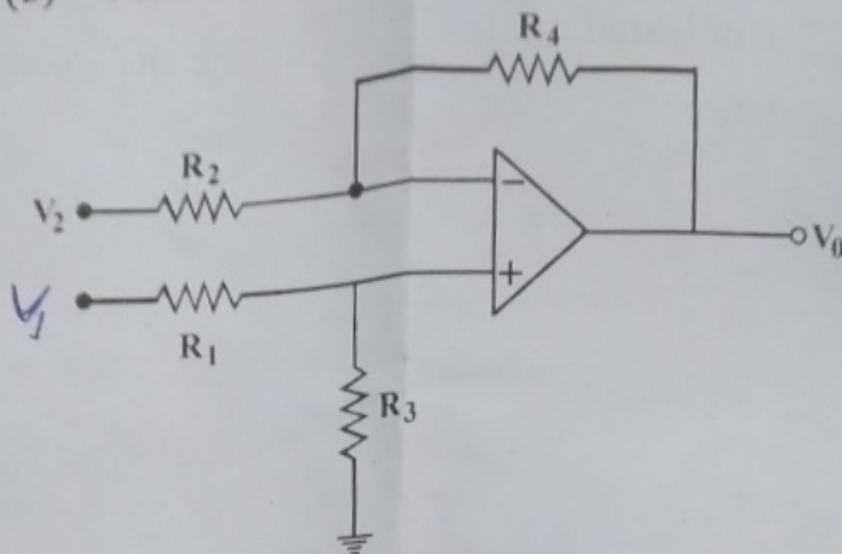


(c) Simplify the following Boolean expression :

(i) $A\bar{B} + \bar{A}B + \bar{A}\bar{B} + AB$

(ii) $A\bar{B}C + \bar{A}BC + ABC$

6. (a) Draw the equivalent circuit of OR, AND, XOR and XNOR gates using NAND gates only.

(b) Find the output voltage V_0 :

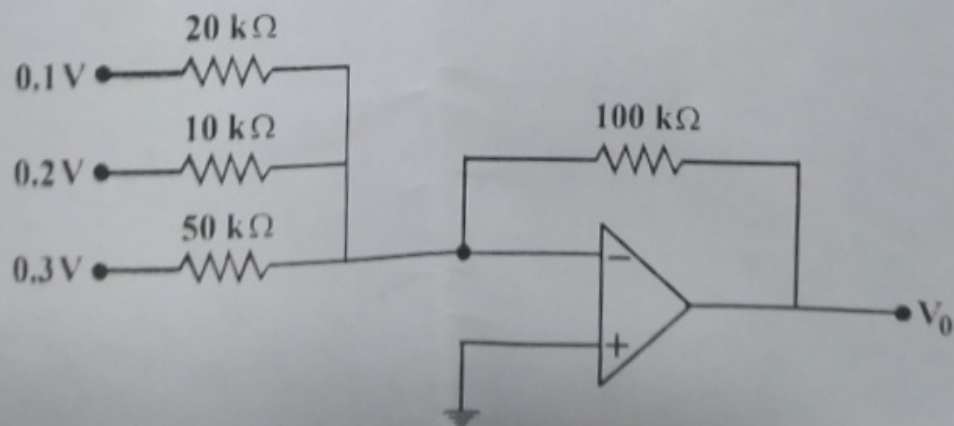

[P.T.O.]

- (c) Explain the term SOP and POS related to Boolean function. Also define the universal gates.
