

S.No. : 59

NEE 4101

No. of Printed Pages : 05

Following Paper ID and Roll No. to be filled in your Answer Book.

PAPER ID : 43301

Roll
No.

1	2	4	0	4	3	3	3	9	2
---	---	---	---	---	---	---	---	---	---

B. Tech. Examination, 2024-25

(Odd Semester)

BASIC ELECTRICAL ENGINEERING

Time : Three Hours]

[Maximum Marks : 60

Note :- Attempt all questions.

SECTION-A

1. Attempt all parts of the following : $8 \times 1 = 8$

- (a) What is the difference between mesh and loop?
- (b) What is the difference between linear and non-linear elements?
- (c) Define impedances.
- (d) Define line voltage.
- (e) What is Lenz's law?


[P. T. O.]

- (f) Define eddy current loss.
- (g) Define slip.
- (h) What is the synchronous speed?

SECTION - B

2. Attempt any two parts of the following : $2 \times 6 = 12$

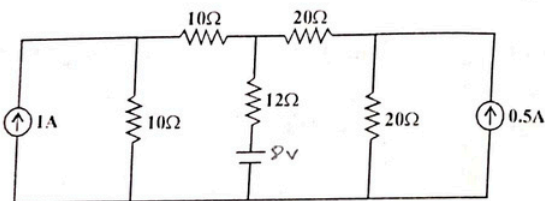- (a) Find the current in $12\ \Omega$ resistance using Thevenin's theorem :




- (b) Explain the measurement of three phase power by two wattmeter method.
- (c) Draw and explain the working of induction type energy meter.
- (d) Why the synchronous meter is not self starting?

SECTION - C

Note :- Attempt all questions. Attempt any two parts from each questions. $8 \times 5 = 40$

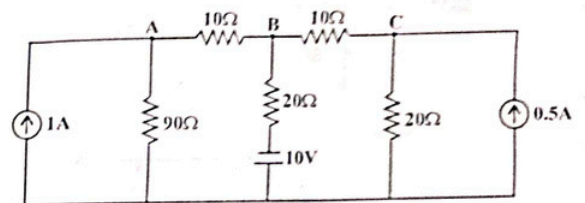- 3. (a) State and explain maximum power transfer theorem to solve network problems and also write two applications.
- (b) Find the current in each element by nodal analysis :



- (c) How is delta connected network converted into equivalent star connected network?
4. (a) An a.c. ckt has four different voltages :
- $$V_1 = 100 \sin 500 t$$
- $$V_2 = 180 \sin (500 t + \pi/3)$$
- $$V_3 = -60 \cos 500 t$$
- $$V_4 = 150 \sin (500 t + \pi/4)$$


what will the equivalent voltage in that circuit also calculates r.m.s. average value.

[P. T. O.]

- (b) For LCR series circuit drive an expression for resonant frequency :

$$f_r = \sqrt{f_1 f_2}$$

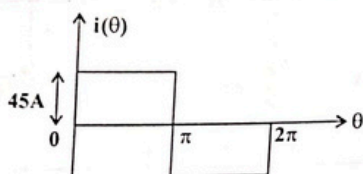- (c) Calculate the r.m.s. and average value of the given waveform :



5. (a) Compare moving iron instrument with dynamometer instrument and which is the best one.
- (b) Derive e.m.f. equation of transformer.
- (c) Compare electrical circuit with magnetic circuit.
6. (a) A 4 pole, 1200 rpm generator with lap wound armature has 65 slots and 12 conductors per slot. The flux per pole is 0.02 wb. Calculate the e.m.f. generated.

- (b) Why the single phase induction motor is not self starting write two methods to start the single phase induction motor?
- (c) Derive the torque equation for D.C. motor.
